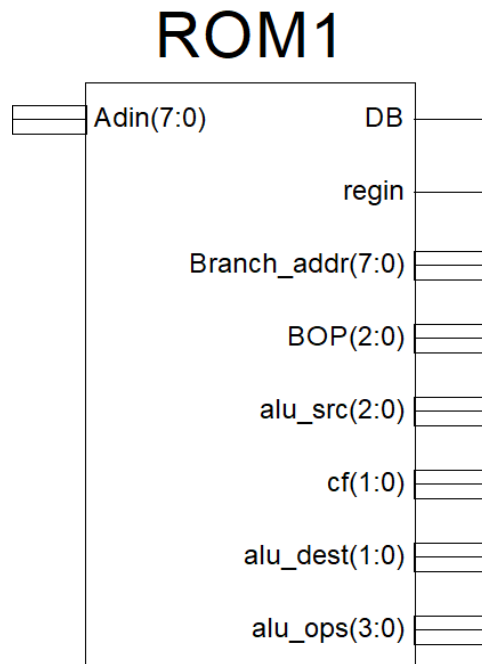


Discussion on each component

ROM: This is where the microcode resides, the ROM is a component used to store data that controls every component of the processor.



VHDL CODE:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity ROM1 is
port(Adin:in std_logic_vector(7 downto 0);
      Branch_addr: out std_logic_vector(7 downto 0);
      DB,regin: out std_logic;
```

```

        BOP ,alu_src :out std_logic_vector(2 downto 0);
        cf,alu_dest:out std_logic_vector(1 downto 0);
        alu_ops:out std_logic_vector(3 downto 0));
end ROM1;

architecture archROM1 of ROM1 is
--microcode for ADD16u-----
constant data1:STD_LOGIC_VECTOR(23 downto 0):="0000000001110100000000001";
constant data2:STD_LOGIC_VECTOR(23 downto 0):="0000000001110000000000000";
constant data3:STD_LOGIC_VECTOR(23 downto 0):="0000000001110100000000011";
constant data4:STD_LOGIC_VECTOR(23 downto 0):="0100000001110000000000000";
constant data5:STD_LOGIC_VECTOR(23 downto 0):="1010000001100011000000001";

type rom_array is array(NATURAL range<>) of STD_LOGIC_VECTOR(23 downto 0);
constant rom:rom_array:=(data1,data2,data3,data4,data5);

begin
process(Adin)
variable j:integer;
variable M: std_logic_vector(23 downto 0);

begin
j:=conv_integer(Adin);
M:=rom(j);
Branch_addr<=M(7 downto 0);
DB<=M(8);
BOP<=M(11 downto 9);
regin<=M(12);
cf<=M(14 downto 13);
alu_ops<=M(18 downto 15);

```

```

alu_src<=M(21 downto 19);
alu_dest<=M(23 downto 22);
end process;
end archROM1;

```

ROM SIMULATION




Explanation:

The ROM moves to the location pointed by the adin [7:0] and outputs the data in the specified location.

In this case adin is “00000100”, so the ROM outputs data in the location “00000100” and branches to Branch location specified in the data, in this case Branch address is “00000000”.

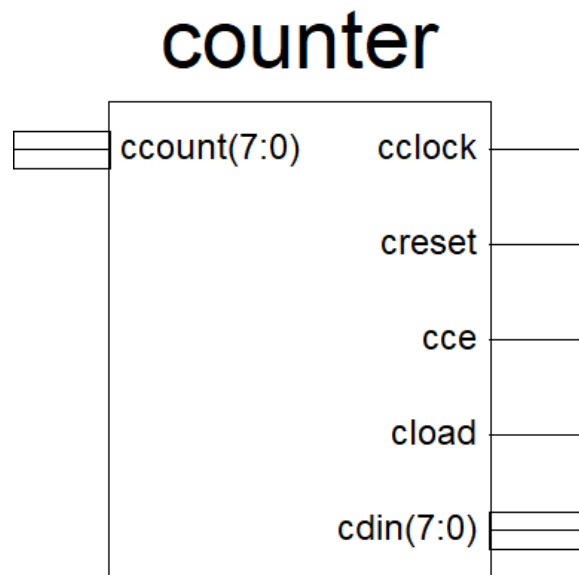COUNTER: The counter is responsible for propagating through the microcode inside the ROM.



VHDL CODE:


```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity counter is
port(cclock,creset,cce,cload:in std_logic;
      cdin:in std_logic_vector(7 downto 0);
      ccount:out std_logic_vector(7 downto 0));
end counter;
architecture arch_counter of counter is
begin
process(cclock,creset)
```

```

variable tmp : std_logic_vector(7 downto 0):=x"00";
begin
    if rising_edge(cclock) then
        if creset='1'then
            tmp:=x"00";
        end if;
        if(cce='0' and cload='0') then
            tmp:=tmp;
        elsif(cce='0' and cload='1') then
            tmp:=cdin;
        elsif(cce='1' and cload='0') then
            tmp:=tmp+1;
        elsif(cce='1' and cload='1') then
            tmp:=cdin;
        end if;
    end if;
    ccount<= tmp;
end process;
end arch_counter;

```

COUNTER SIMULATION

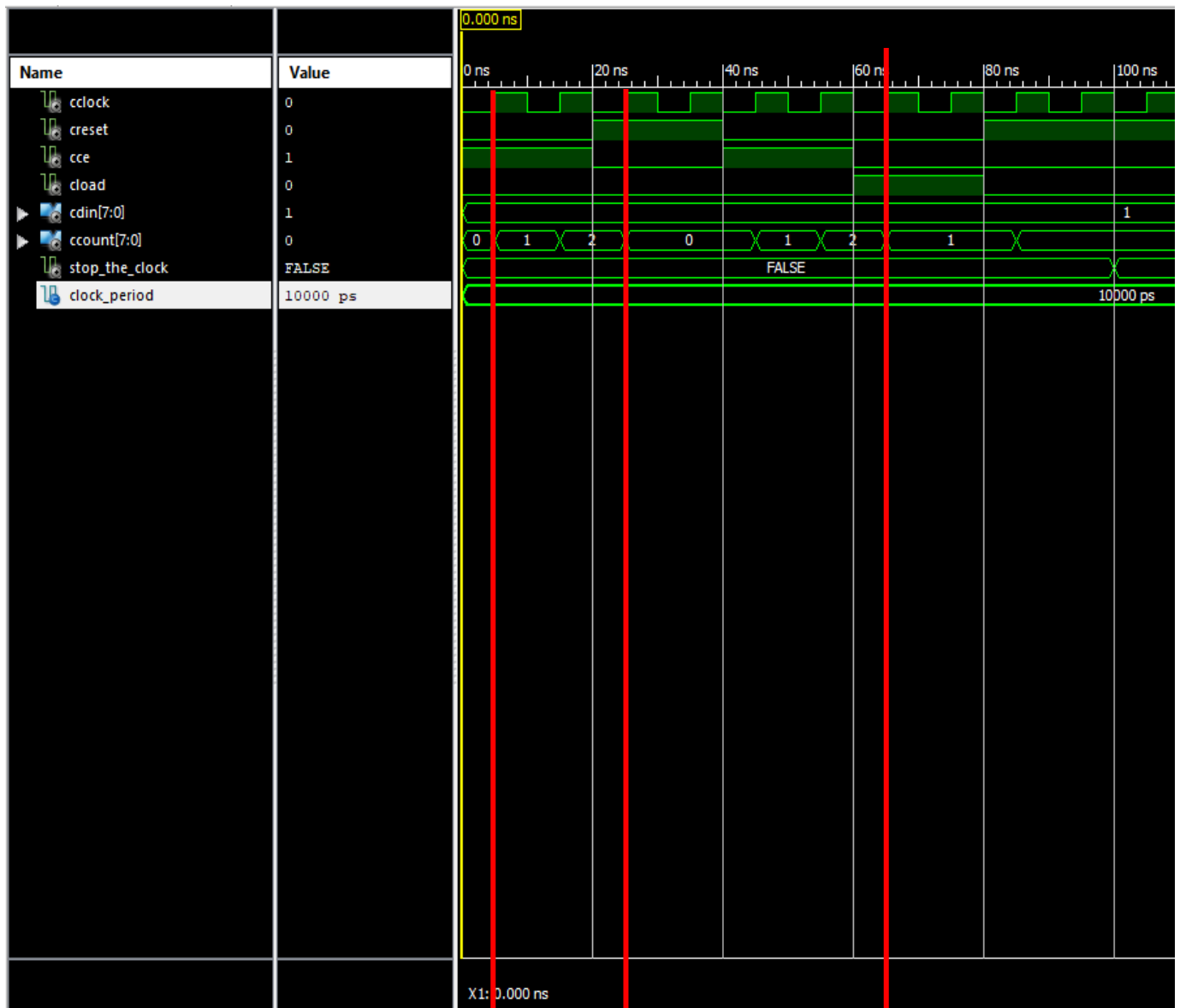


When Count enable is high and Count Load is low, at the rising edge of clock the counter counts

When Count reset is high the count output is zero

When Count enable is low and Count Load is high, at the rising edge of clock cdin is loaded to counter output

BUFFER CONTROL: The Buffer control is a component used to generate control signals to ALU_BUS_CONTROL. i.e. a, b, c, d. based on the input signal DB, Regin.

BUFFER_CONTROL

 


VHDL CODE:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use ieee.std_logic_arith.all;
use ieee.std_logic_unsigned.all;
entity BUFFER_CONTROL is
port(DB,regin :in std_logic;
a,b,c,d :out std_logic);
end BUFFER_CONTROL;
architecture Behavioral of BUFFER_CONTROL is
begin
process(DB,regin)
begin
if(DB='0') and (regin='0') then
a<='0';
```



```
b<='0';
c<='0';
d<='1';
elsif(DB='0') and (regin='1') then
a<='0';
b<='0';
c<='1';
d<='1';
elsif(DB='1') and (regin='0') then
a<='0';
b<='1';
c<='0';
d<='0';
elsif(DB='1') and (regin='1') then
a<='1';
b<='0';
c<='0';
d<='0';
end if;
end process;
end Behavioral;
```


BUFFER CONTROL SIMULATION

 

Regin	DB	a	b	c	d
0	0	0	0	0	1
0	1	0	0	1	1
1	0	0	1	0	0
1	1	1	0	0	0

ALU BUS CONTROL: This component determines the source of data to the Registers. Data can be sent from the ALU output(data_out), Data bus input(data_in), Opcode input(addr). These sources are selected according to the control input signal a,b,d.

ALU_BUS_CNTRL

 


VHDL CODE:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use ieee.std_logic_arith.all;
use ieee.std_logic_unsigned.all;
entity ALU_BUS_CNTRL is
port( data_out,data_in:in std_logic_vector(15 downto 0);
a,b,d:in std_logic;
addr: in std_logic_vector(7 downto 0);
alu_bus:inout std_logic_vector(15 downto 0));
```

```
end ALU_BUS_CNTRL;

architecture Behavioral of ALU_BUS_CNTRL is
begin
process(a,b,d,alu_bus,data_in,data_out,addr)
begin
if b = '1' then
    alu_bus<=data_in;
elsif a = '1' then
    alu_bus<=x"0000";
    alu_bus(7 downto 0)<=addr;
elsif d = '1' then
    alu_bus<=data_out;
else
    alu_bus<=alu_bus;
end if;
end process;
end Behavioral;
```

ALU BUS CONTROL SIMULATION

 


When d='1'.
alu_bus=data_out

When b='1'.
alu_bus=data_in

When a='1'.
alu_bus=addr

ALU/DB to Register: This component determines the destination register to the input ALU_BUS. The destination register is controlled by the control signal Alu_dest.

ALU_DB_TO_REGISTER

 


VHDL CODE:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use ieee.std_logic_arith.all;
use ieee.std_logic_unsigned.all;
entity ALU_DB_TO_REGISTER is
port( ALU_BUS :in std_logic_vector(15 downto 0);
      ALU_DEST :in std_logic_vector(1 downto 0);
      clk :in std_logic;
      regl,rega,regb,regc :out std_logic_vector(15 downto 0):=x"0000");
end ALU_DB_TO_REGISTER;
architecture Behavioral of ALU_DB_TO_REGISTER is
begin
process(ALU_BUS,ALU_DEST,clk)
begin
```

```
if(rising_edge(clk) ) then
if( ALU_DEST = "00")then
rega<=ALU_BUS;
elsif(ALU_DEST = "01")then
regb<=ALU_BUS;
elsif(ALU_DEST = "10")then
regc<=ALU_BUS;
elsif(ALU_DEST = "11")then
regl<=ALU_BUS;
end if;
end if;
end process;
end Behavioral;
```

ALU/DB to Register simulation:

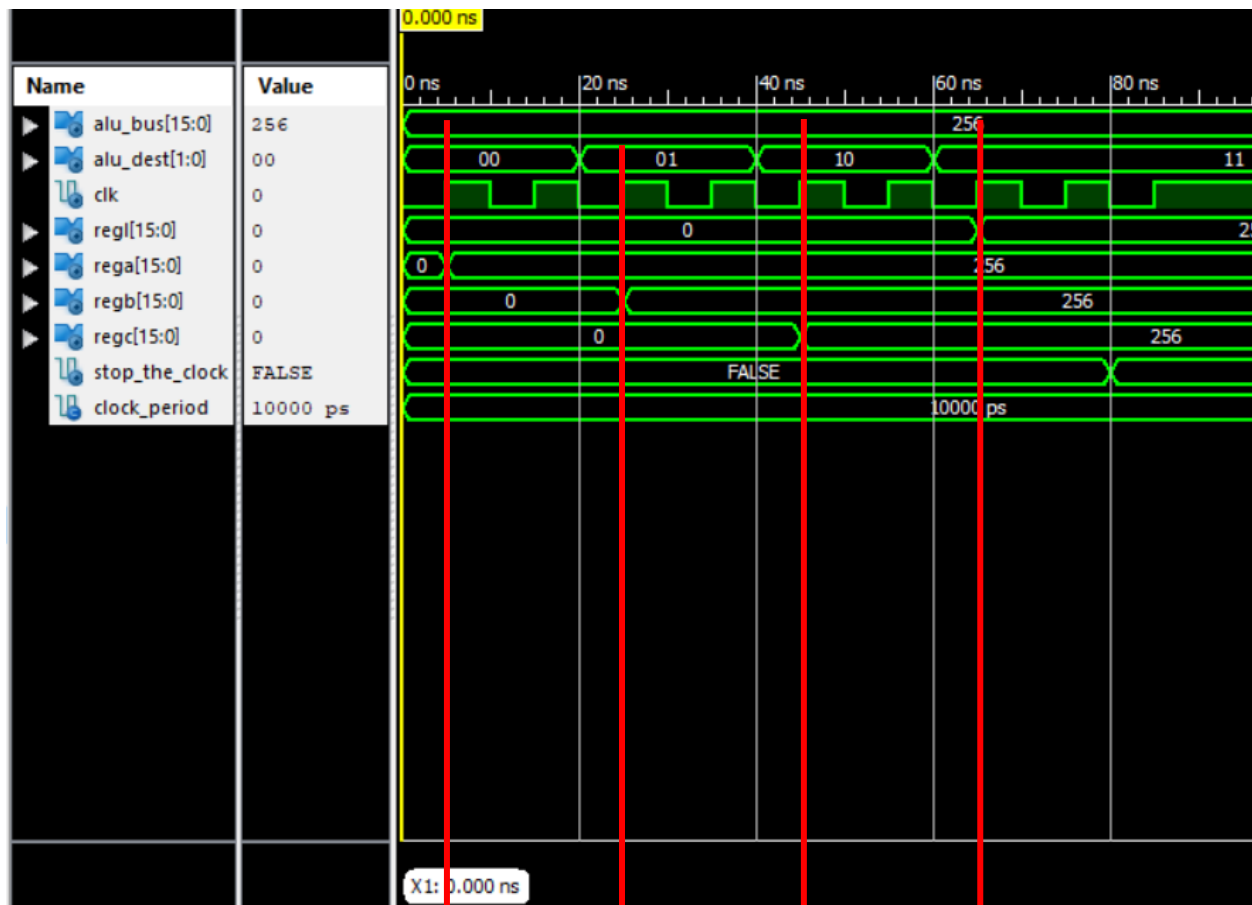

When alu_dest="00",
then output In Reg A


When alu_dest="01",
then output In Reg B

When alu_dest="10",
then output In Reg C

When alu_dest="11",
then output In Reg L

REGISTER to ALU: This component is responsible to control the input data to the ALU. The input data are from four source registers and the Register to ALU component selects any two of the four source registers as ALU input for binary operations, and one of the four source registers for unary operations.

REGISTER_TO_ALU

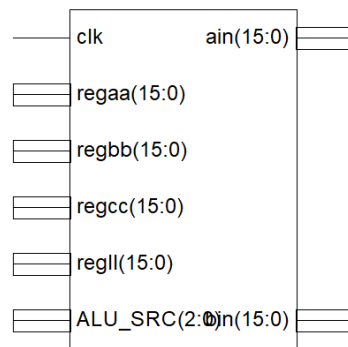

VHDL CODE:

```

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

use ieee.std_logic_arith.all;
use ieee.std_logic_unsigned.all;

entity REGISTER_TO_ALU is
port(regaa,regbb,regcc,regll :in std_logic_vector(15 downto 0);
    ALU_SRC :in std_logic_vector(2 downto 0);
    ain,bin :inout std_logic_vector(15 downto 0);
    clk: in std_logic);
end REGISTER_TO_ALU;
  
```

architecture Behavioral of REGISTER_TO_ALU is

-----decoder-----

component decoder is

port(ALU_SRCd :in std_logic_vector(2 downto 0);

D1,D2,D3:out std_logic;

clk :in std_logic);

end component;

-----mux2_1-----

component mux2_1 is

port(in1_1,in1_2 :in std_logic_vector(15 DOWNTO 0);

s1:in std_logic;

out1:out std_logic_vector(15 DOWNTO 0));

end component;

-----ALL_SIGNALS-----

signal s1,s2,s5 :std_logic;

signal s3,s4,s6 :std_logic_vector(15 downto 0);

begin

G1:decoder port map(ALU_SRC,s1,s2,s5,clk);

G2:mux2_1 port map(regcc,regbb,s1,s3);

G3:mux2_1 port map(regaa,regll,s2,s4);

G4:mux2_1 port map(s3,s4,s5,s6);

G5:mux2_1 port map(s6,s4,ALU_SRC(2),ain);

G6:mux2_1 port map(ain,s3,ALU_SRC(2),bin);

end Behavioral;

---Entity decoder-----

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity decoder is
port(ALU_SRCd :in std_logic_vector(2 downto 0);
D1,D2,D3 :out std_logic;
clk: in std_logic);
end decoder;

architecture archdecoder of decoder is
begin
process(clk,ALU_SRCd)
begin
if(rising_edge(clk))then
    if(ALU_SRCd ="000")then
        D1<='X';
        D2<='0';
        D3<='1';
    elsif(ALU_SRCd ="001")then
        D1<='1';
        D2<='X';
        D3<='0';
    elsif(ALU_SRCd ="010")then
        D1<='0';
        D2<='X';
```

```

    D3<='0';
    elsif(ALU_SRCd ="011")then
    D1<='X';
    D2<='1';
    D3<='1';
    elsif(ALU_SRCd ="100")then
    D1<='1';
    D2<='0';
    D3<='1';
    elsif(ALU_SRCd ="101")then
    D1<='0';
    D2<='0';
    D3<='1';
    elsif(ALU_SRCd ="110")then
    D1<='1';
    D2<='1';
    D3<='1';
    elsif(ALU_SRCd ="111")then
    D1<='0';
    D2<='1';
    D3<='1';
end if;
end if;
end process;
end archdecoder;

```

-----Entity MUX2_1-----

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;


use IEEE.STD_LOGIC_ARITH.ALL;

use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity MUX2_1 is
port(in1_1,in1_2 :in std_logic_vector(15 DOWNT0 0);
sl1:in std_logic;
out1:out std_logic_vector(15 DOWNT0 0));
end MUX2_1;

architecture archMUX2_1 of MUX2_1 is
begin
process(in1_1,in1_2,sl1)
begin
if(sl1='0')then
out1<=in1_1;
elsif(sl1='1')then
out1<=in1_2;
end if;
end process;
end archMUX2_1;
```

REGISTER to ALU simulation

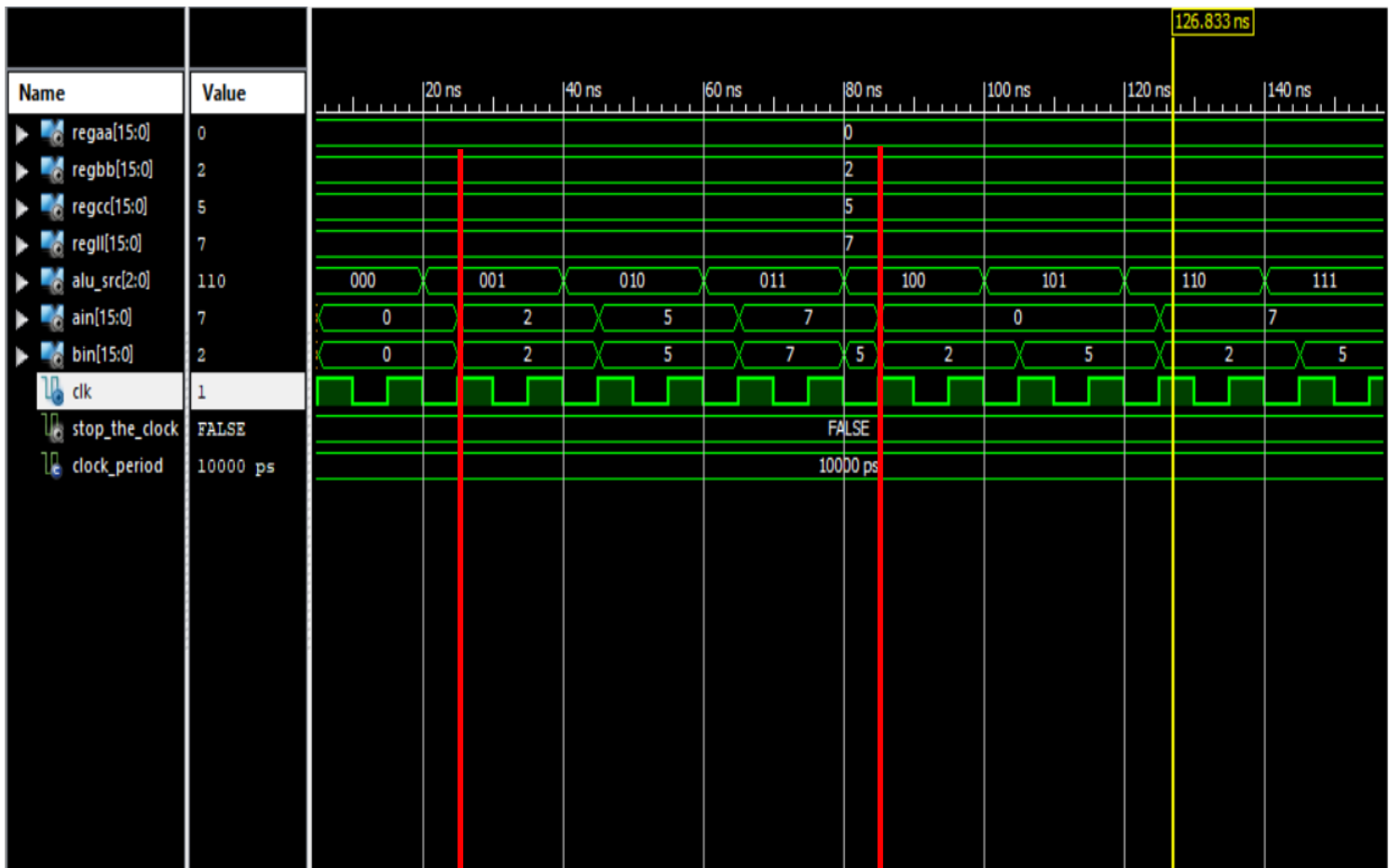

When alu_src="001",
Ain and Bin of ALU = Reg A
Ain=2, Bin=2, for Unary Operation


When alu_src="100",
Ain =Reg A, Bin = Reg B
Ain=0, Bin=2, for Binary Operation

ALU: This component is responsible to perform all the arithmetic and logical operations for the processor. The ALU performs,

Arithmetic ops	Signed, Unsigned, 16-bit, 32-bit
ADD	
SUB	
MULT	
INCR	
DECR	
CLR	

Logical Ops	16-bit, 32-bit
AND	
OR	
NOT	
XOR	

Shift Ops	16-bit, 32-bit
Logical	Signed, Unsigned, 16-bit, 32-bit
Arithmetic	

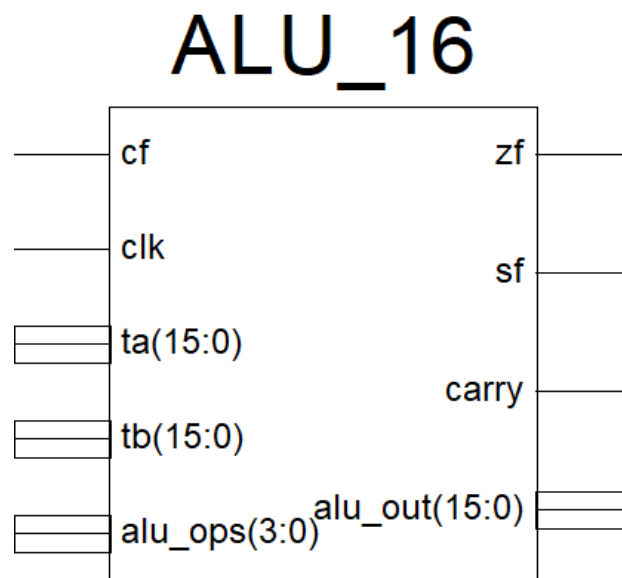

VHDL CODE:

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

use ieee.std_logic_arith.all;

use ieee.std_logic_unsigned.all;

use IEEE.NUMERIC_STD.ALL;


entity ALU_16 is
port(ta,tb :in std_logic_vector(15 downto 0);
cf,clk : in std_logic;
alu_ops:in std_logic_vector(3 downto 0);
zf,sf,carry: out std_logic;
alu_out:out std_logic_vector(15 downto 0));
end ALU_16;


architecture arch_ALU of ALU_16 is
signal temp_aluout :std_logic_vector(15 downto 0):="0000000000000000";
signal xc: std_logic;
begin
process(clk,ta,tb,cf)
begin
if(rising_edge(clk))then
---ADD---
if(alu_ops="0000")then
temp_aluout<=ta+tb;
if(not ta)<tb then xc<='1';end if;
---SUB---
```



```

elseif(alu_ops="0001")then
    temp_aluout<=ta+(not tb)+1;
    if ta<tb then xc<='1';end if;
---AND---
elseif(alu_ops="0010")then
    for i in 0 to 15 loop
        temp_aluout(i)<=ta(i) and tb(i);
    end loop;
---OR---
elseif(alu_ops="0011")then
    for i in 0 to 15 loop
        temp_aluout(i)<=ta(i) or tb(i);
    end loop;
---XOR---
elseif(alu_ops="0100")then
    for i in 0 to 15 loop
        temp_aluout(i)<=ta(i) xor tb(i);
    end loop;
---PASS---
elseif(alu_ops="0101")then
    temp_aluout<=temp_aluout;
---NOT---
elseif(alu_ops="0110")then
    for i in 0 to 15 loop
        temp_aluout(i)<=not ta(i);
    end loop;
---SHLCF---

```

```

elsif(alu_ops="0111")then
    temp_aluout<= ta(14 downto 0) & cf;
    xc<=ta(15);
---SHRCF---
elsif(alu_ops="1000")then
    temp_aluout<= cf & ta(15 downto 1);
    xc<=ta(0);
---INCR----
elsif(alu_ops="1001")then
    temp_aluout<=ta+x"0001";
    if temp_aluout = x"0000" then xc<='1'; end if;
---DECR----
elsif(alu_ops="1010")then
    temp_aluout<=ta-x"0001";
    if temp_aluout = x"FFFF" then xc<='1';end if;
---CLEAR---
elsif(alu_ops="1011")then
    temp_aluout<="0000000000000000";
end if;
alu_out<=temp_aluout(15 downto 0);
if(temp_aluout=x"0000")then
zf<='1';
else
zf<='0';
end if;
if(temp_aluout(15)='1')then
sf<='1';

```

```

else
sf<='0';

end if;

carry<=xc;


end if;

end process;

end arch_ALU;

```

ALU SIMULATION:

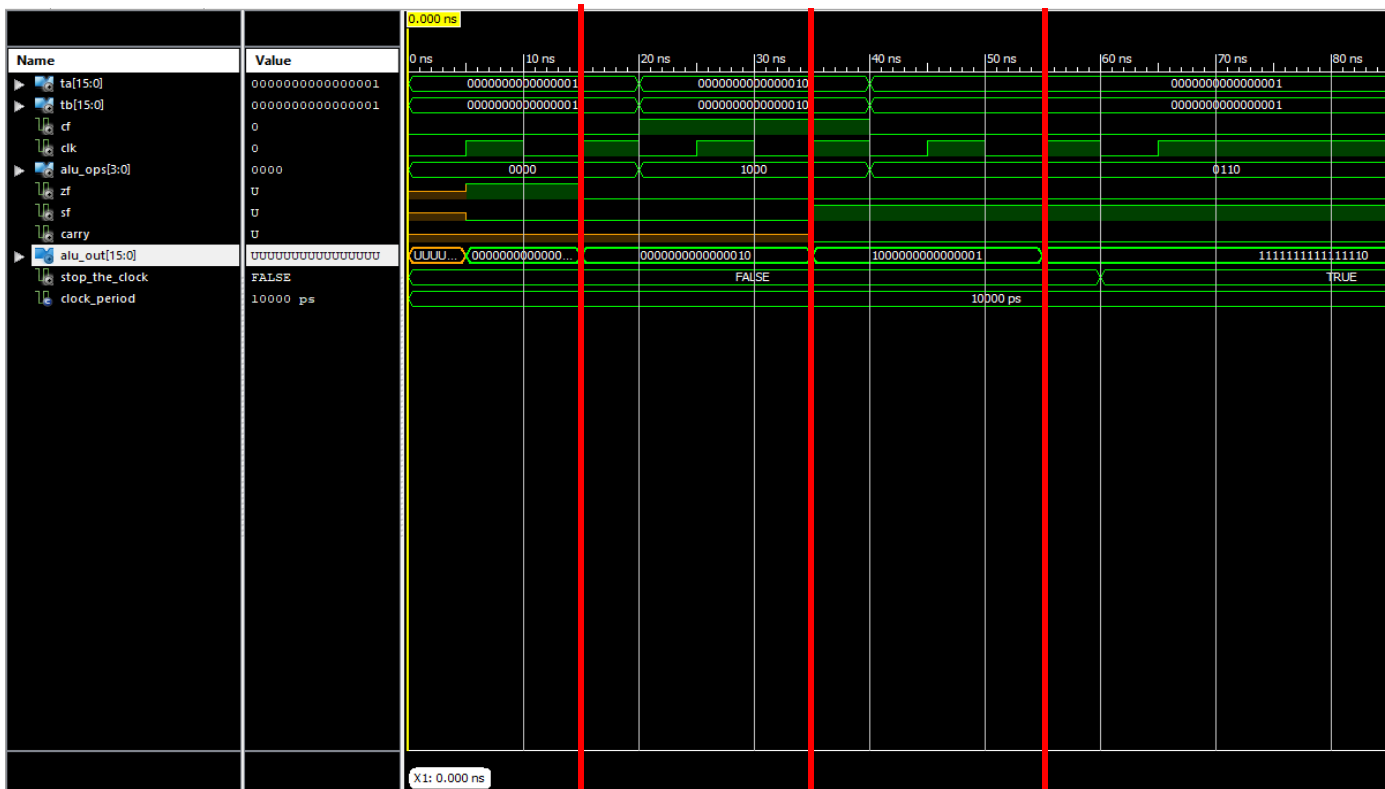


Alu_out= ta+tb, when
Alu_ops="0000"

Alu_out= Shift right
with CF (ta), when
Alu_ops="1000"

Alu_out= not ta, when
Alu_ops="0110"

BRANCH CONTROL: This component determines which branch operation to perform from the microcode. The control signal to the component is the BOP from the Microprogram (ROM).

BRANCH_CNTRL

 

VHDL CODE:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use ieee.std_logic_arith.all;
use ieee.std_logic_unsigned.all;

entity BRANCH_CNTRL is
port(BRDEN,BROP,BRZ,BRP,BRC,BRCF: in std_logic;
BOP: in std_logic_vector(2 downto 0);
CE,LOAD :out std_logic);
end BRANCH_CNTRL;
```

architecture Behavioral of BRANCH_CNTRL is

begin

process(BOP)

begin

if(BOP = "000") then

CE<='1';

LOAD<='0';

elsif(BOP ="001") then

CE<='0';

LOAD<='1';

elsif(BOP ="010") then

CE<=BRDEN;

LOAD<=NOT BRDEN;

elsif(BOP ="011") then

CE<=BROP;

LOAD<=NOT BROP;

elsif(BOP ="100") then

CE<=BRZ;

LOAD<=NOT BRZ;

elsif(BOP ="101") then

CE<=BRP;

LOAD<=NOT BRP;

elsif(BOP ="110") then

CE<=BRC;

LOAD<=NOT BRC;

elsif(BOP ="111") then

CE<=BRCF;


LOAD<=NOT BRCF;

end if;

end process;


end Behavioral;

BRANCH CONTROL SIMULATION

 

BOP (2)	BOP (1)	BOP (0)	
0	0	0	NEXT
0	0	1	BRA
0	1	0	BRDEN
0	1	1	BROP
1	0	0	BRZ
1	0	1	BRP
1	1	0	BRC
1	1	1	BRCF

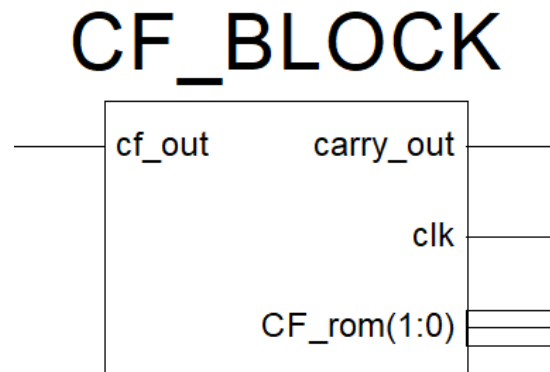CF BLOCK: This component performs the carry flag set, carry, clear, No change operations.



VHDL CODE:


```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use ieee.std_logic_arith.all;
use ieee.std_logic_unsigned.all;
entity CF_BLOCK is
port(CF_rom :in std_logic_vector(1 downto 0);
      carry_out,clk: in std_logic;
      cf_out:inout std_logic);
end CF_BLOCK;
architecture Behavioral of CF_BLOCK is
begin
process(clk,CF_rom,carry_out)
begin
if rising_edge(clk) then
if(CF_rom = "00") then
```

```

        cf_out<=cf_out;
    elsif(CF_rom = "01") then
        cf_out<='1';
    elsif(CF_rom = "10") then
        cf_out<='0';
    elsif(CF_rom = "11") then
        cf_out<=carry_out;
    end if;
end if;
end if;
end process;
end Behavioral;

```

CF SIMULATION

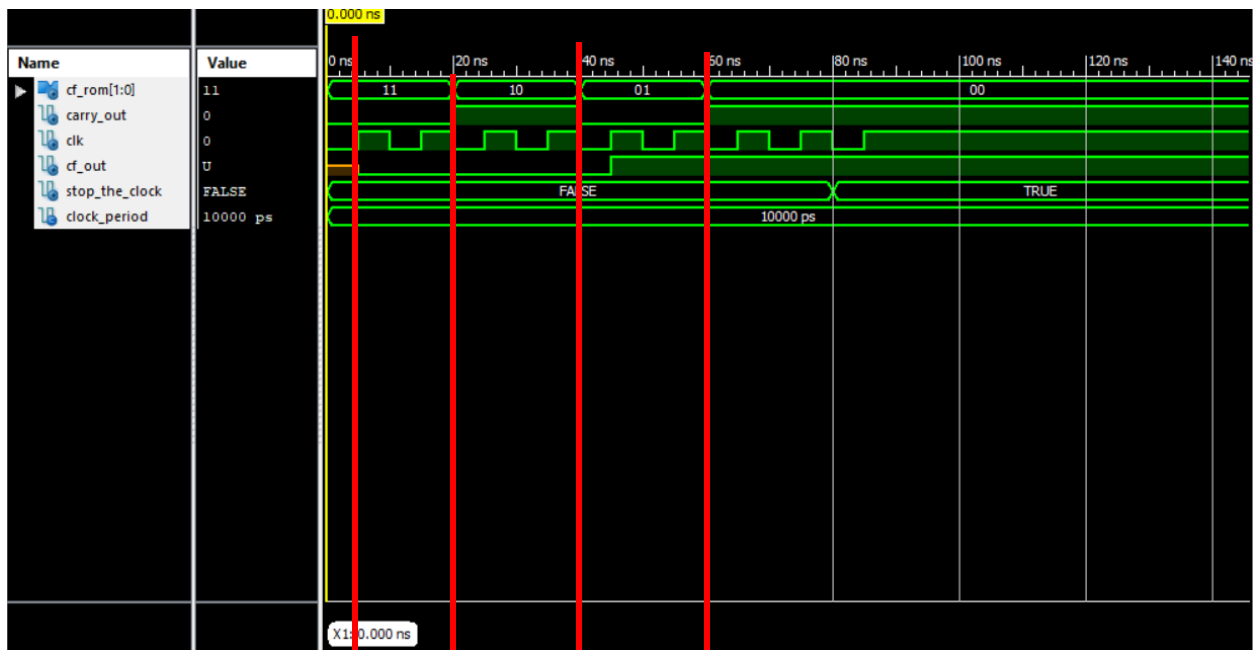


When Bit 14,13 is "11"
CF_OUT=CARRY_OUT

When Bit 14,13 is "01"
CF_OUT=SET (1)

When Bit 14,13 is "00"
CF_OUT=No change

When Bit 14,13 is "10"
CF_OUT=CLR (0)

 ENABLE: To enable ALU output onto the data bus



VHDL CODE:


```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use ieee.std_logic_arith.all;
use ieee.std_logic_unsigned.all;
use IEEE.NUMERIC_STD.ALL;

entity enable is
port(data_in:in std_logic_vector(15 downto 0);
      data_out:inout std_logic_vector(15 downto 0);
      en :in std_logic);
end enable;

architecture Behavioral of enable is
begin
process(en)
begin
if(en = '1')then
data_out<=data_in;
elsif(en = '0')then
data_out<=data_out;
```

```
end if;  
end process;  
end Behavioral;
```

ENABLE SIMULATION

 

MICROCODE

ADD 32 u

Offset	Alu_dest	Alu_src	Alu_ops	Cf	Reg_in	Bop	Db	Addr	Description
10	XX	XX	XX	NC	DB	BRDBN	IN	10	Wait for 1st low 16-bit
11	L	XX	XX	NC	DB	NEXT	IN	XX	DB to L
12	XX	XX	XX	NC	DB	BRDBN	IN	12	Wait for 1st high 16-bit
13	A	XX	XX	NC	DB	NEXT	IN	XX	DB to A
14	XX	XX	XX	NC	DB	BRDBN	IN	14	Wait for 2 nd low 16-bit
15	B	XX	XX	NC	DB	NEXT	IN	XX	DB to B
16	XX	XX	XX	NC	DB	BRDBN	IN	16	Wait for 2 nd high 16-bit
17	C	XX	XX	CLR	DB	NEXT	IN	XX	DB to C
18	B	LB	ADD	CAR	ALU	NEXT	OUT	XX	B+L+CF to B
19	C	AC	ADD	CAR	ALU	BRA	OUT	00	C+A+CF to C & go to "00"

ADD 16 s

Offset	Alu_dest	Alu_src	Alu_ops	Cf	Reg_in	Bop	Db	Addr	Description
20	XX	XX	XX	NC	DB	BRDBN	IN	20	Wait for 1 st data
21	A	XX	XX	NC	DB	NEXT	IN	XX	DB to A
22	XX	XX	XX	NC	DB	BRDBN	IN	22	Wait for 2 nd data
23	B	XX	XX	NC	DB	BRDBN	IN	XX	DB to B
24	C	AB	XOR	CLR	ALU	BRP	IN	26	If AB>0 go to “26” Else next
25	A	AB	ADD	CAR	ALU	BRA	OUT	00	A+B+C F to A& go to “00”
26	A	AB	ADD	CAR	ALU	NEXT	OUT	XX	A+B+C F to A & next
27	C	AC	XOR	NC	ALU	BRP	OUT	00	If AC>0 go to “00” Else next
28	X	X	XX	NC	ALU	BRA	OUT	F0	Overflow, go to “F0”

MULT 16u

Offset	Alu_dest	Alu_src	Alu_ops	Cf	Reg_in	Bop	Db	Addr	Description
30	PASS	PASS	PASS	NC	DB	BRDBN	IN	30	Wait for m'ier
31	C	C	PASS	NC	DB	NEXT	IN	XX	DB to C (m'ier)
32	PASS	PASS	PASS	NC	DB	BRDBN	IN	32	Wait for m'end
33	A	A	PASS	NC	DB	NEXT	IN	XX	DB to A (m'end)
34	PASS	PASS	PASS	NC	DB	BROP	OUT	34	Wait for op
35	L	L	PASS	NC	DB	NEXT	OUT	10	counter OP to L(counte r)
36	B	B	CLR	CLR	ALU	NEXT	IN	XX	Clear B
37	L	L	DECR	CLR	ALU	BRZ	IN	3E	If L-1=0 goto "3E"
38	B	B	SHLCF	CAR	ALU	NEXT	IN	XX	B to B(14:0)+'0', CF=B(15)
39	C	C	SHLCF	CAR	ALU	BRC	IN	3B	C□C(14:0)+CF,C F=C(15) If Carry=1 goto "3B"
3A	L	L	PASS	CLR	ALU	BRA	IN	37	Clear CF, goto "37"
3B	B	AB	ADD	CAR	ALU	BRC	IN	3D	B to A+B If Carry=1 goto "3D"
3C	C	C	PASS	CLR	ALU	BRA	IN	37	Clear CF, goto "37"
3D	C	C	INCR	CLR	ALU	BRA	IN	37	C+1 to C, goto "37"
3E	L	L	PASS	CLR	ALU	BRA	IN	3E	HOLD

ABS 32 s

Offset	Alu_des t	Alu_src	Alu_ops	Cf	Reg_in	Bop	Db	Addr	Description
40	XX	XX	XX	NC	DB	BRDB N	IN	40	Wait for 1 st data
41	A	XX	XX	NC	DB	NEXT	IN	XX	DB to A
42	XX	XX	XX	NC	DB	BRDB N	IN	42	Wait for 2 nd data
43	B	XX	XX	NC	DB	NEXT	IN	XX	DB to B
44	L	XX	CLR	NC	ALU	NEXT	OUT	XX	Clear L
45	C	B	PASS	NC	ALU	BRP	OUT	00	B to C, If C>0 goto "00"
									Else next
46	B	B	NOT	NC	ALU	NEXT	OUT	XX	~B to B
47	A	A	NOT	CLR	ALU	NEXT	OUT	XX	~A to A
48	A	A	INC	CAR	ALU	NEXT	OUT	XX	A+1 to A
49	B	LB	ADD	CAR	ALU	BRA	OUT	00	B+L+C F to B& goto "00"